 


Moore State Machine

In Moore machine, output only depends on the present state. It is independent of current input.

1. Non-Overlapping Moore State Machine



In this type of sequence detector does not allow overlap, but resets itself to the start state when the sequence has been detected.

For example, after the initial sequence 1101 has been detected, the detector with no overlap resets and starts searching for the initial 1 of the next sequence.

Design Code

```
`timescale 1ns / 1ps
module seq_1010(
    //Global Signals
    input i_clock,
    input i_reset,
    //Button
    input i_btn,
    //LED
    output o_led
) ;
//Local Parameters
localparam [2:0] S0=0, S1=1, S2=2, S3=3, S4=4;

//Internal Registers or wire declarations
reg [2:0] state, next_state;

//Reset Condition
always@(posedge i_clock) begin
    if(i_reset)
        state<=3'b000;
    else
```

```

always@(*) begin
    //Store the state
    next_state = state;

    //State machine
    case(state)
        S0: next_state <= i_btn ? S1:S0;
        S1: next_state <= i_btn ? S1:S2;
        S2: next_state <= i_btn ? S3:S0;
        S3: next_state <= i_btn ? S1:S4;
        S4: next_state <= i_btn ? S1:S0;    //Non overlapping
    //    S4: next_state <= i_btn ? S3:S0;    //Overlapping
    endcase

end

assign o_led = (state == S4) ? 1 : 0;
endmodule

```

Testbench Code

```

`timescale 1ns / 1ps

module seq_1010_tb;

    //Internal Registers/Wires
    reg clk, rst, din;
    wire dout;

    always
        #5 clk = ~clk;

    initial begin

        clk = 0;
        rst=1;
        din=0;

        #35 rst = 0;
        #20 din = 1;
        #20 din = 0;
        #20 din = 1;
        #20 din = 0;
        #20 din = 1;
        #20 din = 0;
        #20 din = 0;
        #20 din = 1;
        #20 din = 0;
        #20 din = 1;
        #20 din = 0;
        #20 din = 1;

        #40 $stop;

    end

end


//initial begin
//    $dumpfile("dump.vcd");
//    $dumpvars(0);
// end

//Instantiation
seq_1010 uut(
    .i_clock(clk),
    .i_reset(rst),
    .i_btn(din),
    .o_led(dout)
);


endmodule

```

Output Waveform:

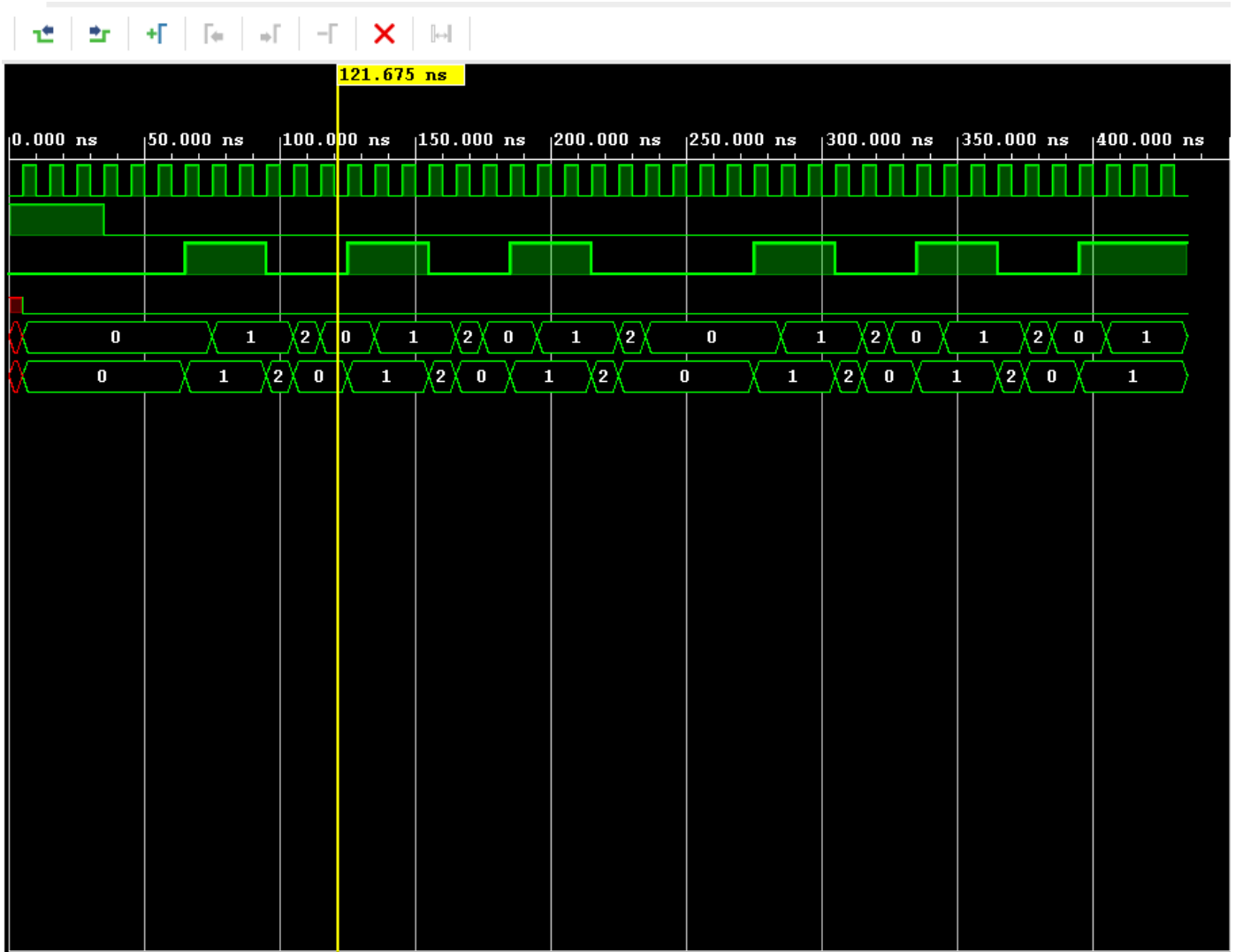

2. Overlapping Moore State Machine

 

In this type of sequence detector allows overlap, the final bits of one sequence can be the start of another sequence.

For example, will be an 1101 sequence detector. It raises an output of 1 when the last 4 binary bits received are 1101.


Design Code

```
module seq_1010(  
    //Global Signals  
    input i_clock,  
    input i_reset,  
    //Button  
    input i_btn,  
    //LED  
    output o_led  
);  
//Local Parameters  
localparam [2:0] S0=0, S1=1, S2=2, S3=3, S4=4;  
  
//Internal Registers or wire declarations  
reg [2:0] state, next_state;  
  
//Reset Condition  
always@(posedge i_clock) begin  
    if(i_reset)  
        state<=3'b000;  
    else  
        state<=next_state;  
end  
  
always@(*) begin  
    //Store the state  
    next_state = state;  
  
    //State machine  
    case(state)  
        S0: next_state <= i_btn ? S1:S0;  
        S1: next_state <= i_btn ? S1:S2;  
        S2: next_state <= i_btn ? S3:S0;  
        // S3: next_state <= i_btn ? S1:S4;  
        S4: next_state <= i_btn ? S1:S0; //Non overlapping  
        S4: next_state <= i_btn ? S3:S0; //Overlapping  
    endcase  
  
end  
  
assign o_led = (state == S4) ? 1 : 0;  
endmodule
```

Testbench Code

```
`timescale 1ns / 1ps  
  
module seq_1010_tb;  
  
    //Internal Registers/Wires  
    reg clk, rst, din;  
    wire dout;  
  
    always  
    #5 clk = ~clk;  
  
    initial begin  
  
        clk = 0;  
        rst=1;  
        din=0;  
  
        #35 rst = 0;  
        #20 din = 1;  
        #20 din = 0;  
        #20 din = 1;  
        #20 din = 0;  
        #20 din = 1;  
        #20 din = 0;  
        #20 din = 0;  
        #20 din = 1;  
        #20 din = 0;  
        #20 din = 1;  
        #20 din = 0;  
        #20 din = 1;  
  
        #40 $stop;  
    end  
  
    //initial begin  
    // $dumpfile("dump.vcd");  
    // $dumpvars(0);  
    // end  
  
    //Instantiation  
    seq_1010 uut(  
        .i_clock(clk),  
        .i_reset(rst),  
        .i_btn(din),  
        .o_led(dout)  
    );  
  
endmodule
```


Output Waveform

 

Mealy State Machine

In mealy machine, output depends on the present state and current input.

1. Non-Overlapping Mealy State Machine

 

In a non-overlapping sequence detector, the last bit of one sequence does not become the first bit of the next sequence. For example:

Input :0110101011001

Output:0000100010000

Design code

```
`timescale 1ns / 1ps

module seq_1010_mealy(
    //Global Signals
    input    i_clock,
    input    i_reset,
    //Button
    input    i_btn,
    //LED
    output   o_led
);
    //Local Parameters
    localparam [2:0] S0=0, S1=1, S2=2, S3=3;

    //Internal Registers or wire declarations
    reg [2:0] state, next_state;

    //Reset Condition
    always@(posedge i_clock) begin
        if(i_reset)
            state<=3'b000;
        else
            state<=next_state;
    end

    always@(*) begin
        //Store the state
        next_state = state;

        //State machine
        case(state)
            S0: next_state <= i_btn ? S1:S0;
            S1: next_state <= i_btn ? S1:S2;
            S2: next_state <= i_btn ? S3:S0;
            S3: next_state <= i_btn ? S1:S0;    //Non overlapping
            // S3: next_state <= i_btn ? S3:S0; //Overlapping
        endcase
    end

    always@(posedge i_clock) begin
        if (i_reset)
            o_led <= 0;
        else begin
            if (~i_btn & (state == S3))
                o_led <= 1'b1;
            else
                o_led <= 1'b0;
        end
    end
endmodule
```

Testbench Code

```
`timescale 1ns / 1ps

//initial begin
//  $dumpfile("dump.vcd");
//  $dumpvars(0);
// end

module seq_1010_tb;

//Internal Registers/Wires
reg clk, rst, din;
wire dout;

//Instantiation
seq_1010 uut(
.i_clock(clk),
.i_reset(rst),
.i_btn(din),
.o_led(dout)
);

endmodule

always
#5 clk = ~clk;


initial begin

    clk = 0;
    rst=1;
    din=0;


    #35 rst = 0;
    #20 din = 1;
    #20 din = 0;
    #20 din = 1;
    #20 din = 0;
    #20 din = 1;
    #20 din = 0;
    #20 din = 0;
    #20 din = 1;
    #20 din = 0;
    #20 din = 1;
    #20 din = 0;
    #20 din = 1;

    #40 $stop;
end
```

Output Waveform

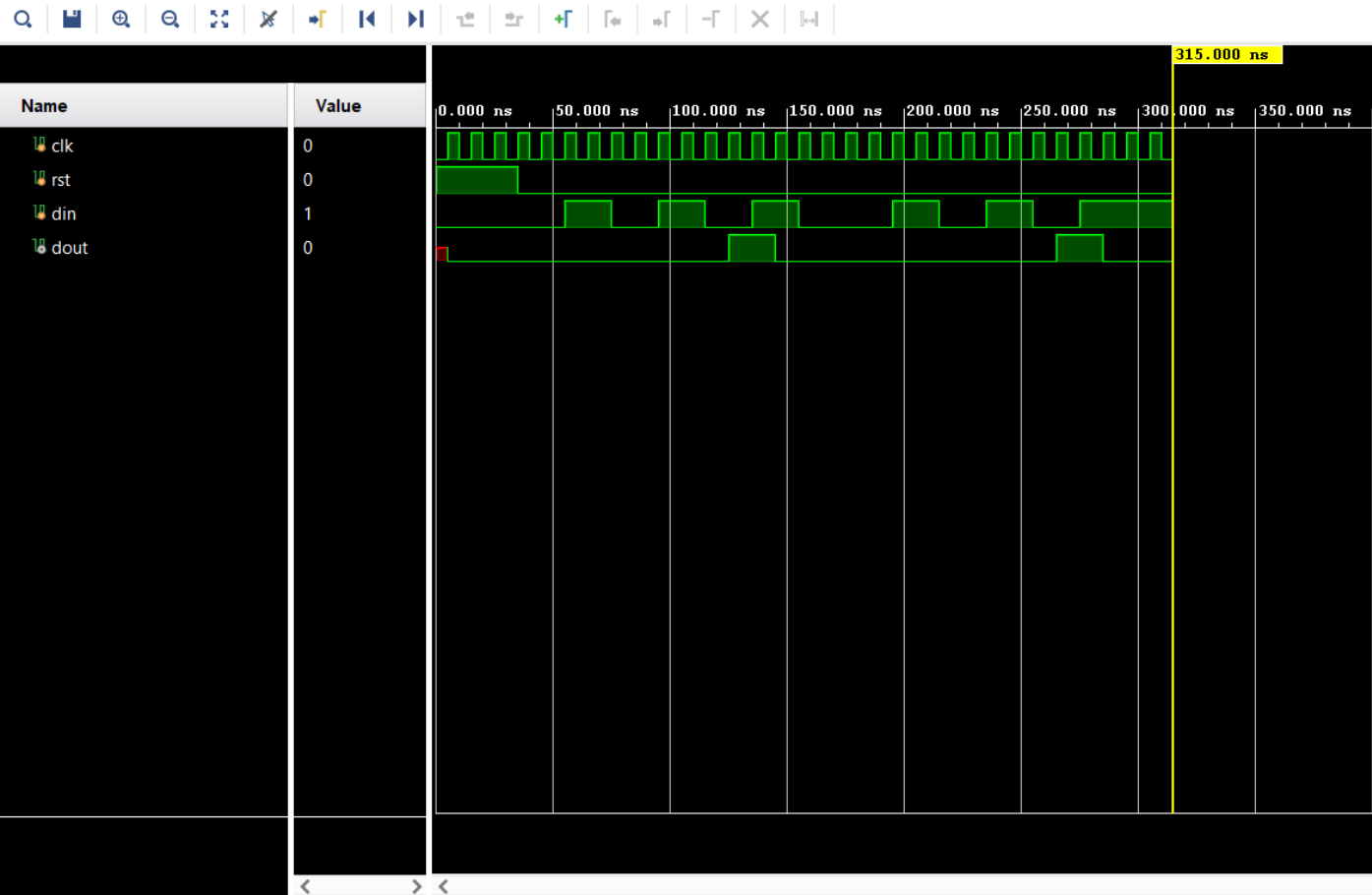

2. Overlapping Mealy State Machine

 

In an overlapping sequence detector, the last bit of one sequence becomes the first bit of the next sequence. For example:

Input :0110101011001

Output:0000101010000

Design Code

```
`timescale 1ns / 1ps

module seq_1010_mealy(
    //Global Signals
    input    i_clock,
    input    i_reset,
    //Button
    input    i_btn,
    //LED
    output reg o_led
);
//Local Parameters
localparam [2:0] S0=0, S1=1, S2=2, S3=3;

//Internal Registers or wire declarations
reg [2:0] state, next_state;

//Reset Condition
always@(posedge i_clock) begin
    if(i_reset)
        state<=3'b000;
    else
        state<=next_state;
end

always@(*) begin
    //Store the state
    next_state = state;

    //State machine
    case(state)
        S0: next_state <= i_btn ? S1:S0;
        S1: next_state <= i_btn ? S1:S2;
        S2: next_state <= i_btn ? S3:S0;
        // S3: next_state <= i_btn ? S1:S0; //Non overlapping
        S3: next_state <= i_btn ? S1:S2; //Overlapping
    endcase
end

always@(posedge i_clock) begin
    if (i_reset)
        o_led <= 0;
    else begin
        if (~i_btn & (state == S3))
            o_led <= 1'b1;
        else
            o_led <= 1'b0;
        end
    end
end
endmodule
```


Testbench Code

```
`timescale 1ns / 1ps

//initial begin
// $dumpfile("dump.vcd");
// $dumpvars(0);
// end

module seq_1010_tb;

//Internal Registers/Wires
reg clk, rst, din;
wire dout;

//Instantiation
seq_1010 uut(
.i_clock(clk),
.i_reset(rst),
.i_btn(din),
.o_led(dout)
);

endmodule

always
#5 clk = ~clk;

initial begin

clk = 0;
rst=1;
din=0;

#35 rst = 0;
#20 din = 1;
#20 din = 0;
#20 din = 1;
#20 din = 0;
#20 din = 1;
#20 din = 0;
#20 din = 0;
#20 din = 1;
#20 din = 0;
#20 din = 1;
#20 din = 0;
#20 din = 1;

#40 $stop;

end
```

Output Waveform

